



This is the Dlopper, a control circuit.  
It outputs gates and control voltage due to light differentials.



1n4001



10uF  
polarised  
cap



1uF  
MLCC  
cap



**B25k**



BC547/8/9