

This is the Dlopper, a control circuit. It outputs gates and control voltage due to light differentials.

♦ BC547 **○○○** B100k **○○** 100uF polcap **○**----**○** 1n4001